

# Phy482 Hw5 Prob 4 Wood

February 16, 2018

```
In [1]: import matplotlib.pyplot as plt
        from math import *
        from math import pi


In [2]: w = 0.0
        dw = 0.1
        wf = 100.0

        R = 1.0
        L = 1.0

        frequency = []
        VRatio = []

        while w < wf:
            Vratio = R/sqrt(R**2+w**2*L**2)
            w = w + dw
            frequency.append(w)
            VRatio.append(Vratio)

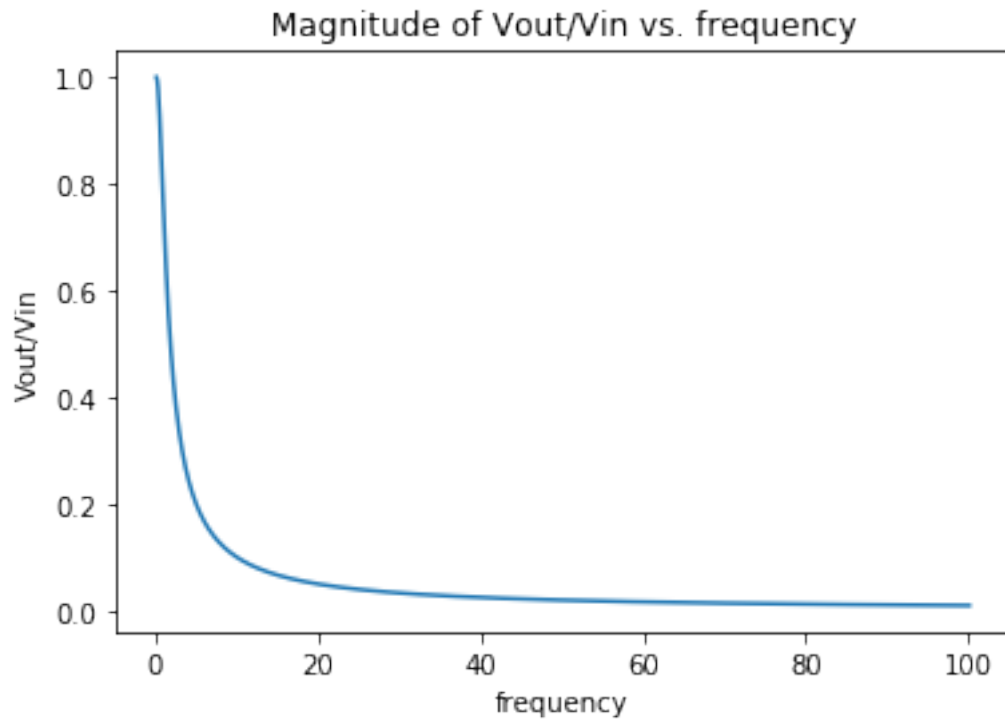        plt.plot(frequency, VRatio)
        plt.xlabel('frequency')
        plt.ylabel('Vout/Vin')
        plt.title('Magnitude of Vout/Vin vs. frequency')
        plt.show()
```



Thus, it looks like the resistor is a low-pass filter, which I already expected from my written homework.

In [3]: `w = 1.0`

```
t = 0.0
dt = 0.1
tf = 100.0
```

```
time = []
Vin = []
```

```
R = 1.0
L = 1.0
```

```
dk = 1.0
kf = 100.0
```

```
while t < tf:
    Vin = 0.0
    k = 1.0
```


```
    while k < kf:
        Vin = Vin + (4/pi)*(sin((2*k-1)*w*t))/(2*k-1)
        k = k + dk
```

```

t = t + dt
time.append(t)
VIn.append(Vin)

plt.plot(time, VIn)
plt.xlabel('time')
plt.ylabel('Vin')
plt.title('Vin vs. time')
plt.show()

```

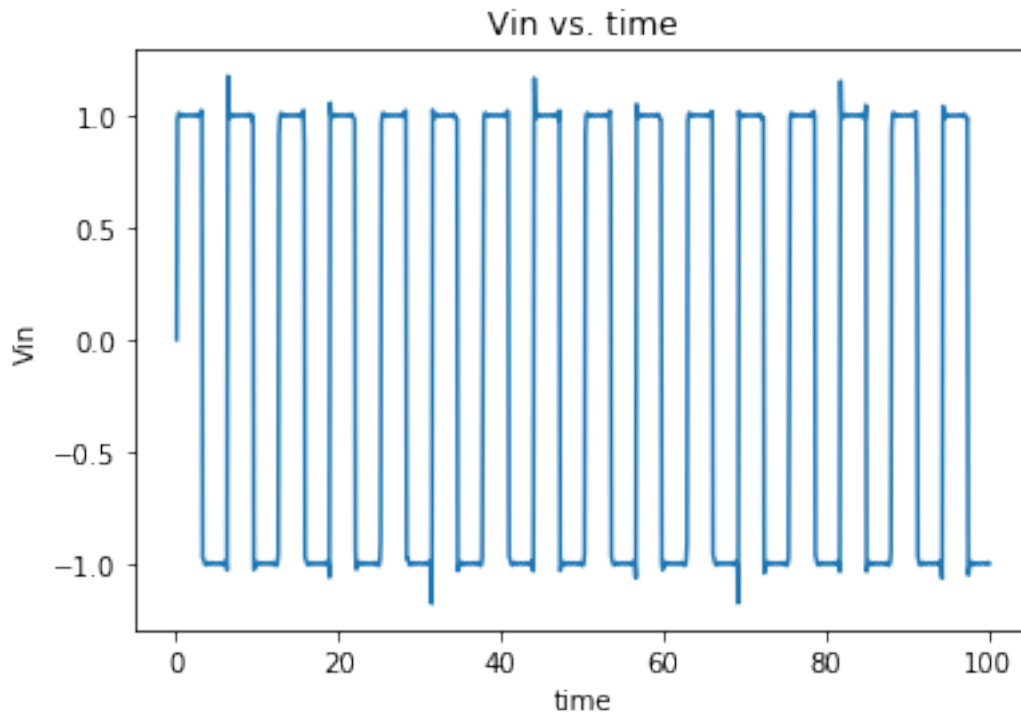

I think  $V_{out}$  should look similar to  $V_{in}$  but shifted (and possibly a different amplitude). I can't figure out how to find  $V_{out}$  though. I don't think phasors work simply here since it's a complicated sum. I think it works to say  $V_{out} = V_{in} - L(dI/dt)$  but I don't know much about  $I$ . I can't figure out what the hint means, that "All the equations are linear, so if the input square wave is constructed from the sum of sinusoidal functions, what does the output look like?" I don't know which equations are linear, so I'm not sure what this tells me.